

# Lecture 03

# Logic Gates

ECE09 – Digital Electronics: Logic Circuit and Switching Theory


Engr. Zoren P. Mabunga, M.Sc


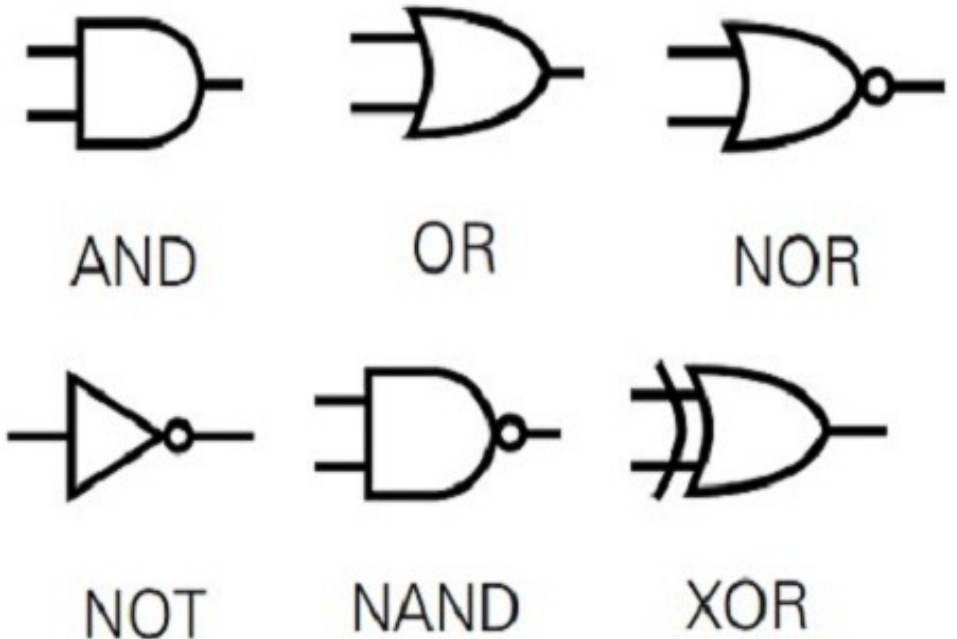
# Definition of Logic Gate

---

- A logic gate is an electronic circuit **which makes logic decision.**
- It has one output and one or more inputs.
- It is the building blocks from which most of the digital systems are made are built up.
- These gates are available today in the form of various IC families. (TTL, ECL, MOS, CMOS)



# Positive and Negative Logic

---

- In computing systems, the number symbols 0 and 1 represent two possible states of a circuit or device.
- The main point is to represent two opposite conditions by 0 and 1.


**Positive Logic** - the more positive of the two voltage levels represent logic 1.

**Negative Logic** - the more negative of the two voltage levels represent logic 1.

# Positive and Negative Logic

- In positive logic, a 1 represents
  - An ON circuit
  - A CLOSED circuit
  - A HIGH voltage
  - A PLUS sign
  - A TRUE statement
- In negative logic, a 1 represents
  - An OFF circuit
  - A OPEN circuit
  - A LOW voltage
  - A MINUS sign
  - A FALSE statement

# The OR gate

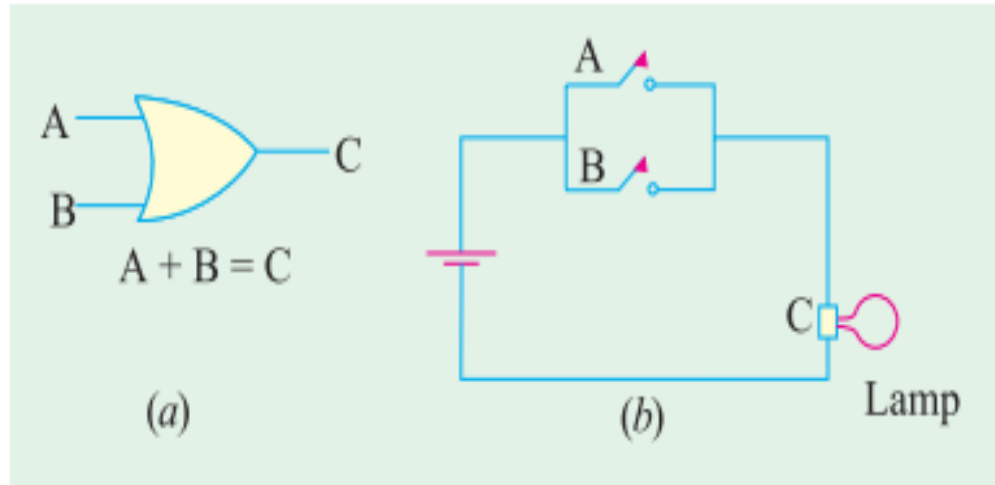

An OR gate is equivalent to a parallel circuit in its logic function.


A truth table may be defined as a table which gives the output state for all possible input combinations.

# Diode OR gate


1. When  $A$  is at +5V,  $D_1$  is forward-biased and hence conducts. The circuit current flows *via*  $R$  dropping 5V across it. In this way, point  $X$  achieves potential of +5 V.
2. When + 5V is applied to  $B$ ,  $D_2$  conducts causing point  $X$  to go to +5 V.
3. When both  $A$  and  $B$  are +5V, the drop across  $R$  is 5V because voltages of  $A$  and  $B$  *are in parallel*.

Again, point  $X$  is driven to +5 V.

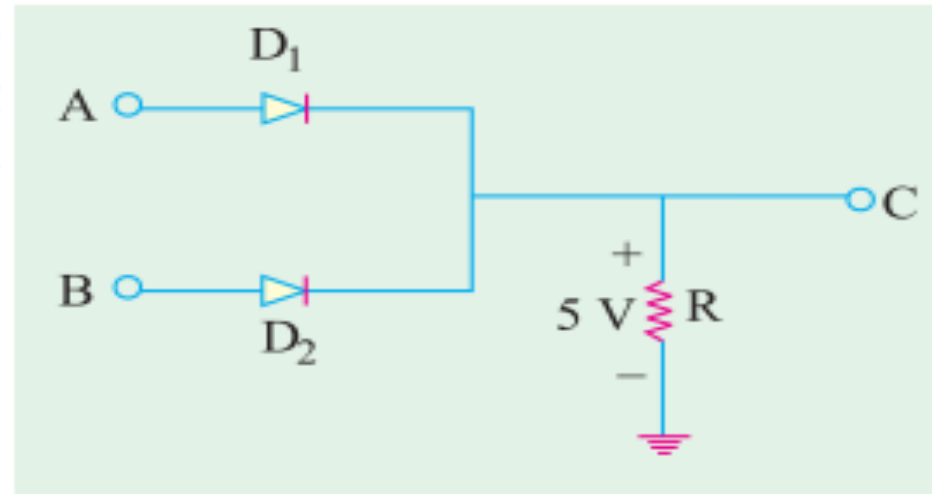4. Obviously, when there is no voltage either at  $A$  or  $B$ , output  $X$  remains 0.



# Transistor OR Gate

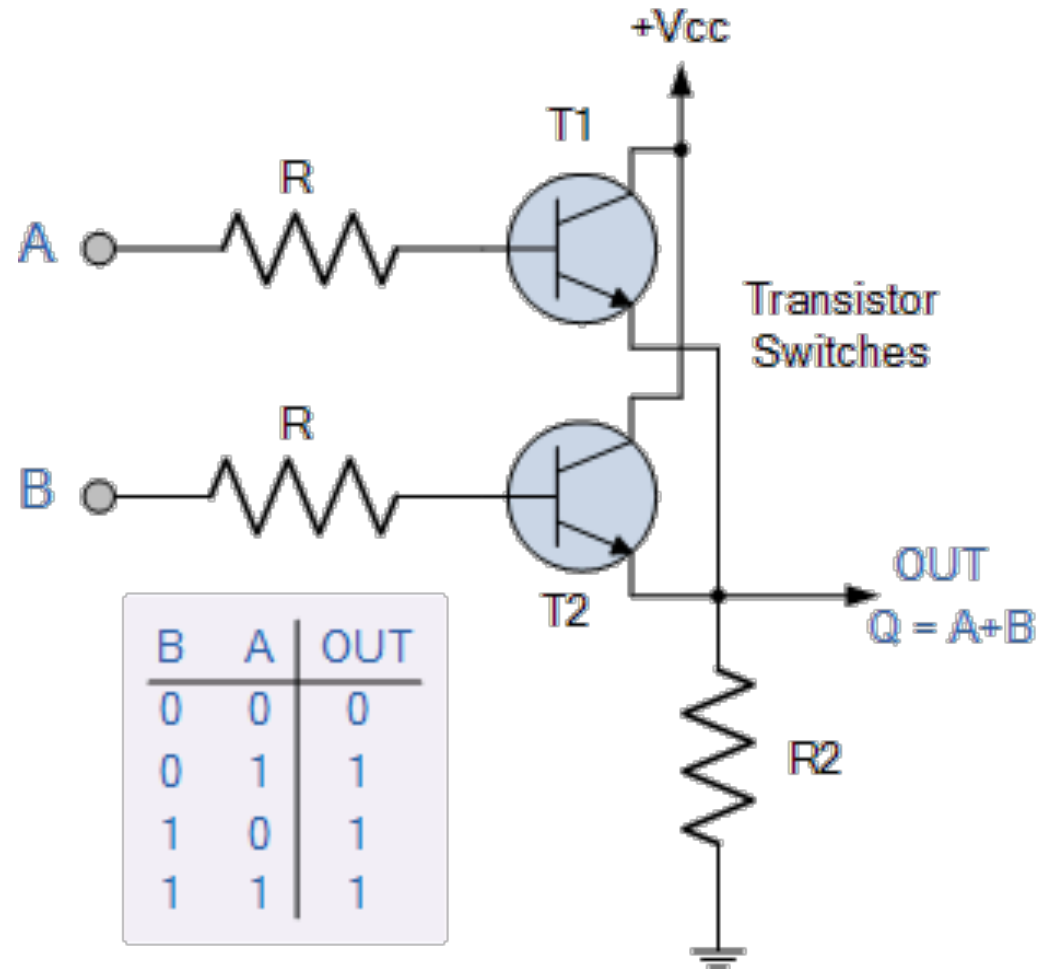

# OR gate operation

- OR gate performs logical addition.

$$\begin{array}{l} 0 + 0 = 0 \\ 0 + 1 = 1 \\ 1 + 0 = 1 \\ 1 + 1 = 1 \end{array}$$

$$1 + 1 = 2 \quad \text{— decimal addition}$$

$$1 + 1 = 10 \quad \text{— binary addition}$$

$$1 + 1 = 1 \quad \text{— OR addition}$$

We can put the above *OR* laws in more general terms

$$A + 1 = 1$$

$$A + 0 = A$$

$$A + A = A \quad \text{— not } 2A$$

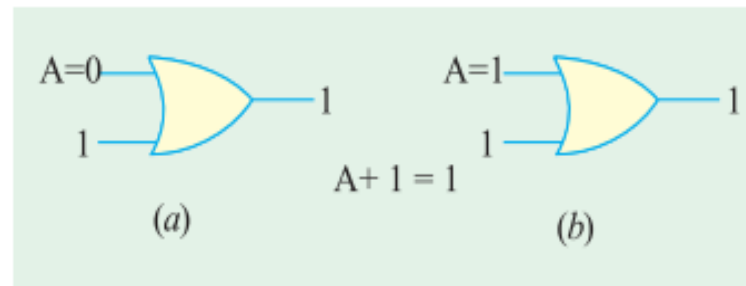



Fig. 70.6



# AND gate

## Logic Operation

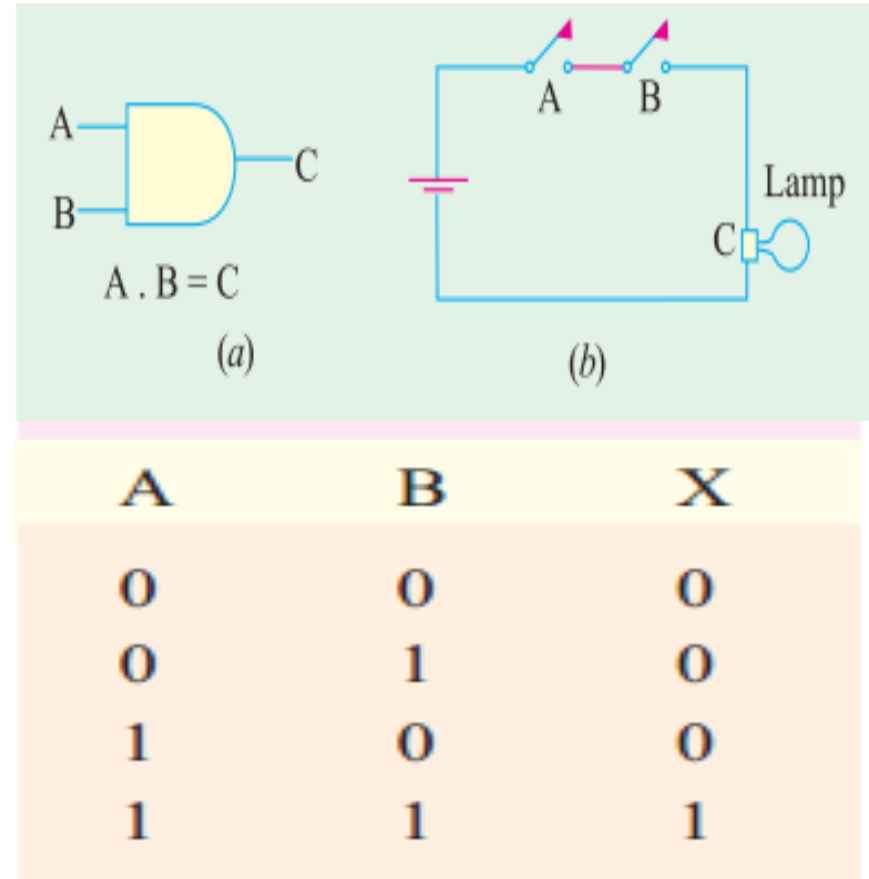
1. The *AND* gate gives an output only **when all its inputs are present**.
  2. The *AND* gate has a 1 output when both *A* **and** *B* are 1. Hence, this gate is an **all-or-nothing** gate whose output occurs only when all its inputs are present.
  3. In True/False terminology, the output of an *AND* gate will be **true** only if **all its inputs are true**. Its output would be false if **any of its inputs is false**.
- The AND gate symbolizes logical multiplication.




# Diode AND gate

1. When  $A$  is at 0 V, diode  $D_1$  conducts and the supply voltage of +5 V drops across  $R$ . Consequently, point  $N$  and hence point  $X$  are driven to 0 V. Therefore, the output  $C$  is 0.
2. Similarly, when  $B$  is at 0 V,  $D_2$  conducts thereby driving  $N$  and hence  $X$  to ground.
3. Obviously, when both  $A$  and  $B$  are at 0 V, both diodes conduct and, again, the output  $X$  is 0.
4. There is no supply current and hence no drop across  $R$  **only when both  $A$  and  $B$  are at +5 V**. Only in that case, the output  $X$  goes to supply voltage of +5 V.

Fig. 70.15

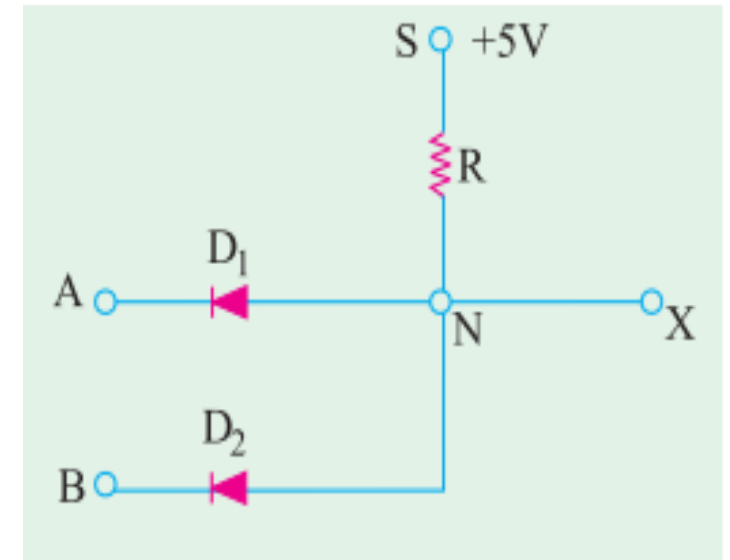


# Transistor AND circuit

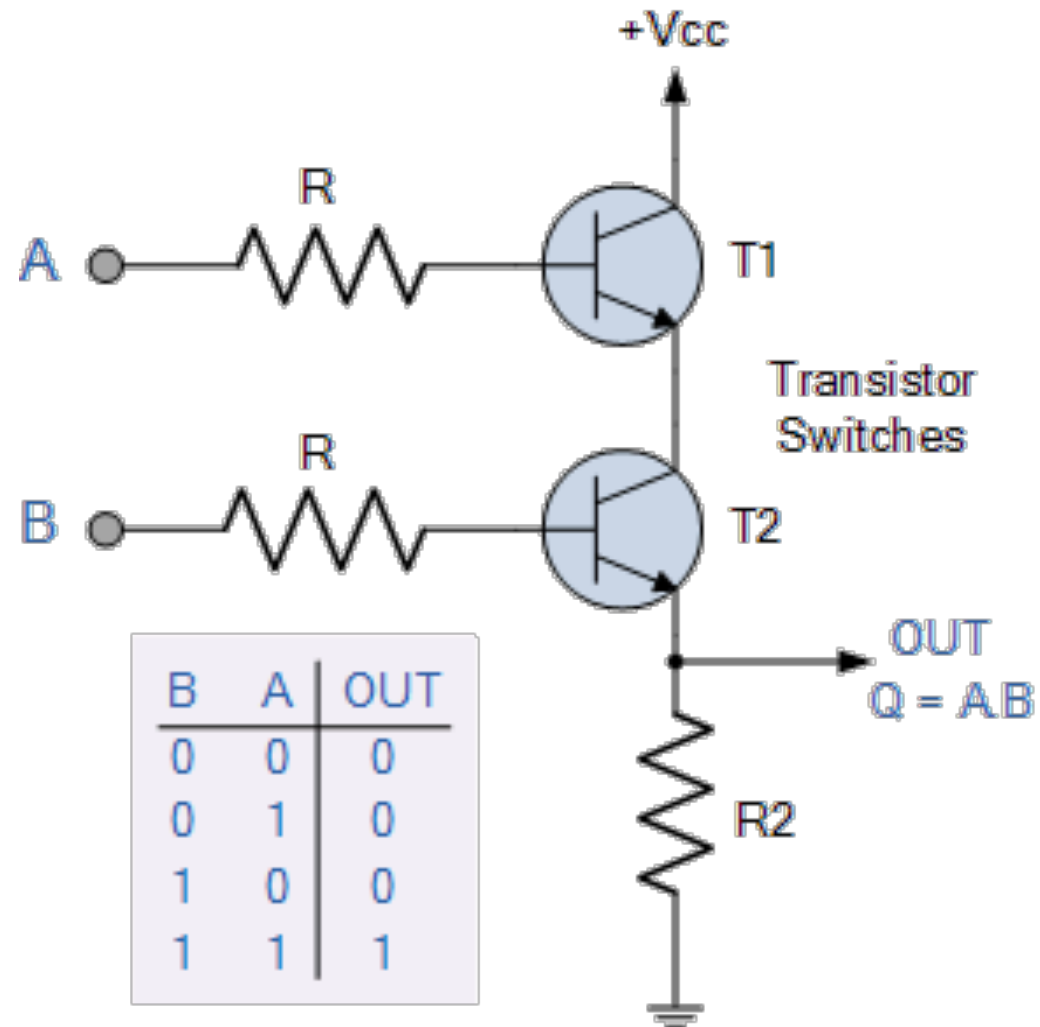

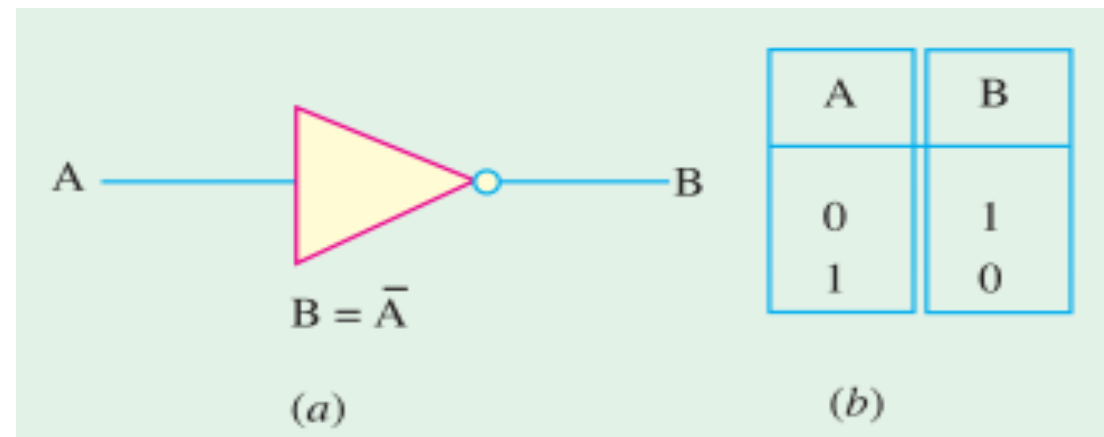
# NOT gate

- Its output is not the same as its input.
- Also called as *inverter*
- Has one input and one output




# Equivalent Circuit of NOT gate

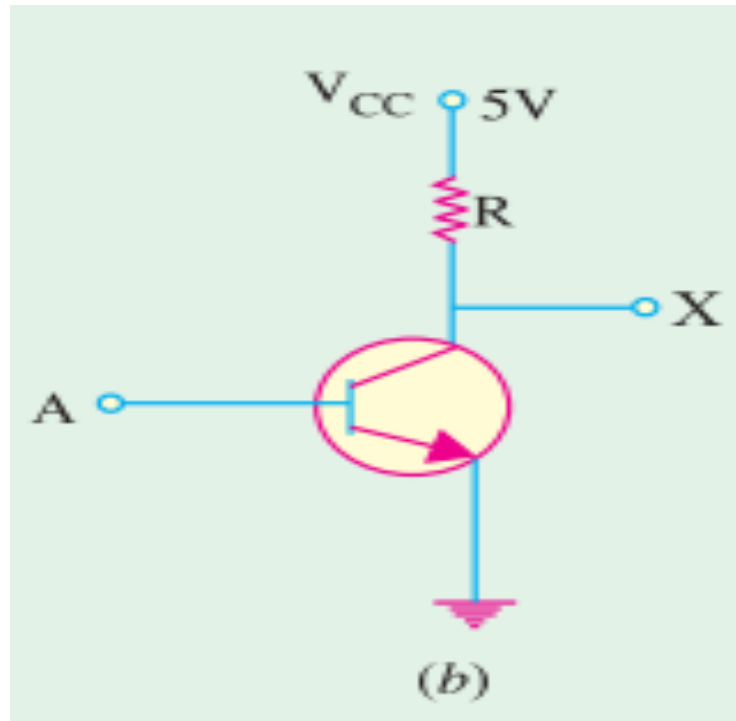



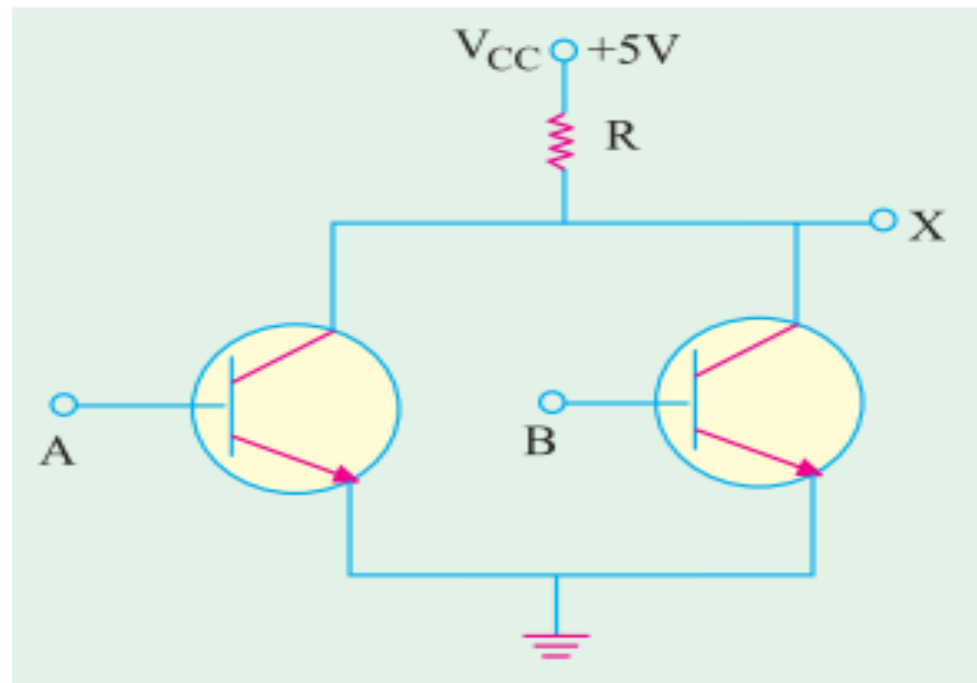
# NOR gate

- A NOR gate is the reverse of OR gate.
- Universal gate



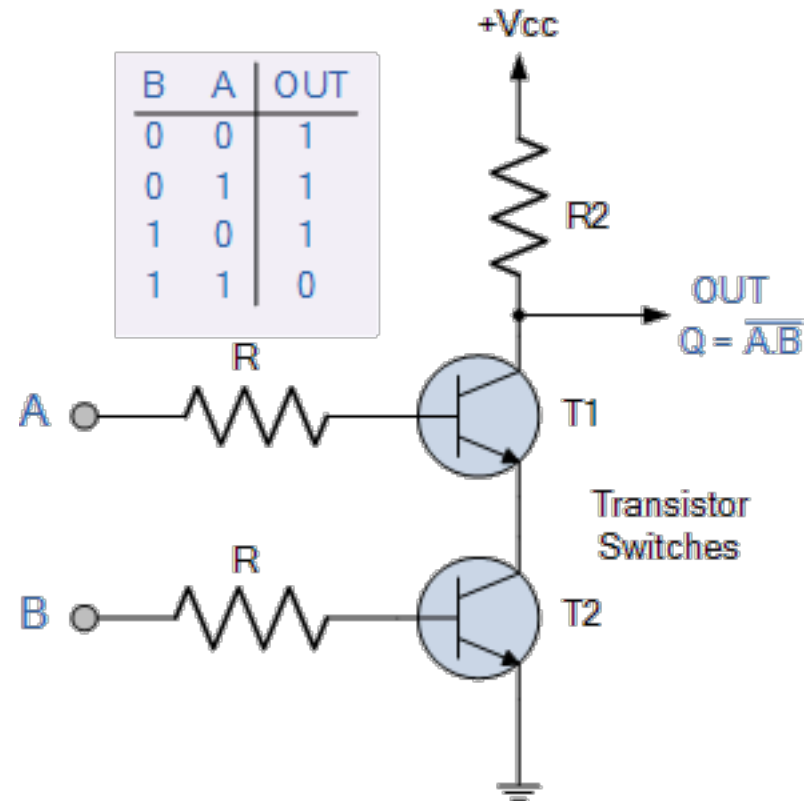
# NAND gate


- Gives an output of 1 if its both inputs are not 1.
- Universal gate



# XOR and XNOR gate

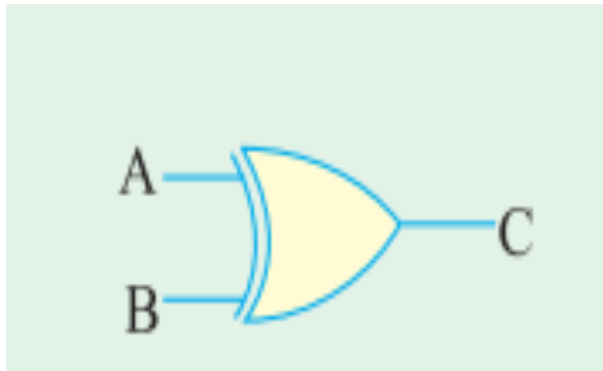


A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

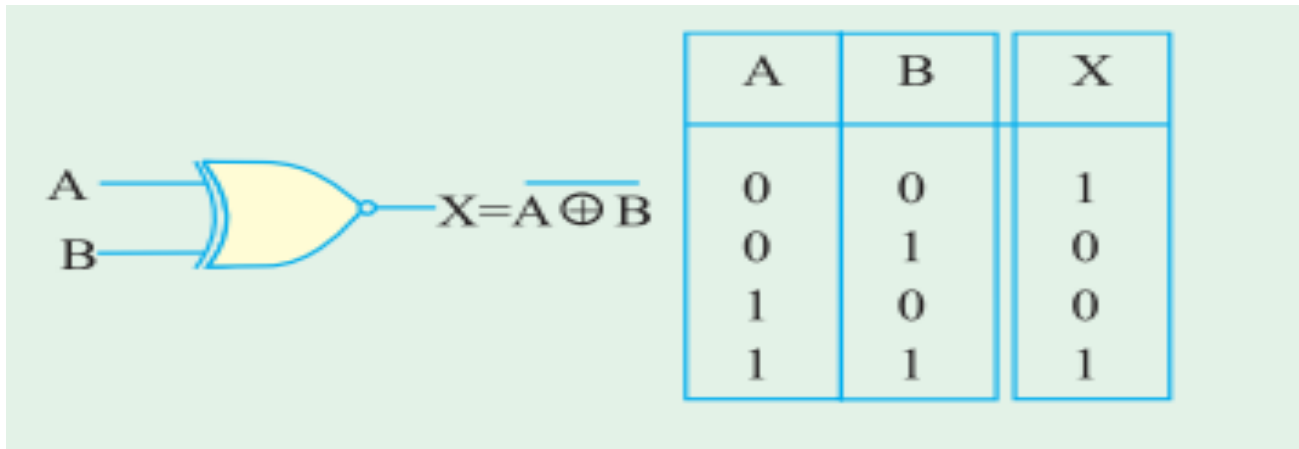


A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

# Summary of Logic Gates

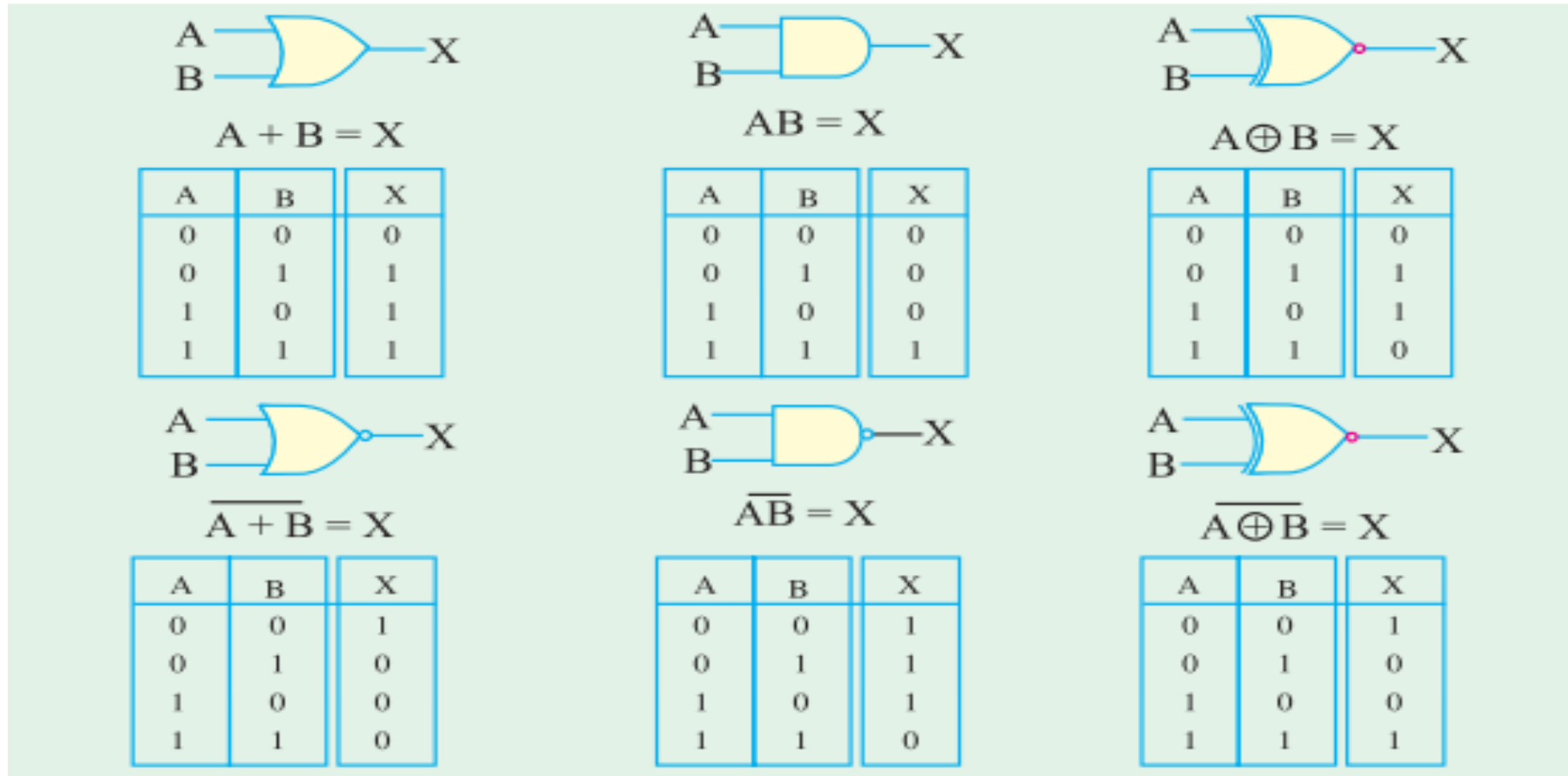

# Sample Problems

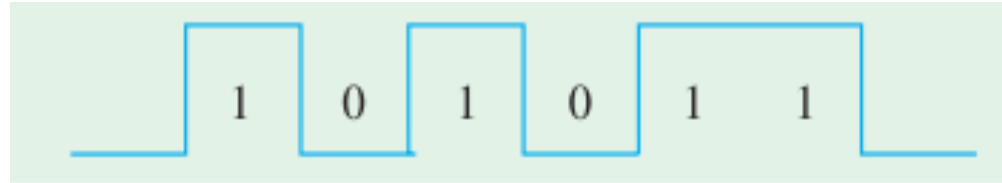1. An electrical signal is expressed as 101011. If the signal is applied to a NOT gate, what would be the output signal?



2. Two electrical signals represented by A = 101101 and B = 110101 are applied to 2-input AND gate. Sketch the output signal and the binary number it represents.




# Sample Problems

1. Design a logic hardware based on the Boolean expression  $(A + \bar{B}C)$ .
2. Design a logic circuit whose output is given by the Boolean expression  $(A + B)\overline{AB}$ .

# Sample Problems


1. Fig. 70.59 shows a 2-input AND gate with waveforms A and B. Sketch the resulting output waveform.

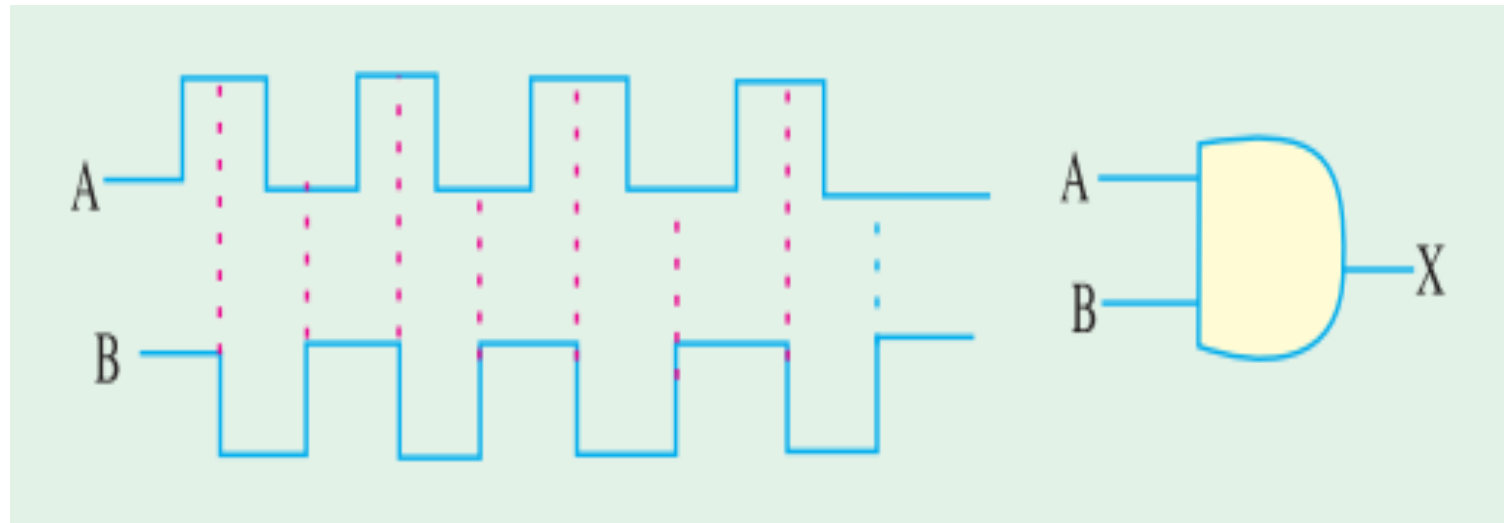

**Fig. 70.59**

# Sample Problems

1. The waveforms A and B are applied as an input to XOR gate and XNOR gate as shown in Fig. 70.71. Determine the output waveforms of these logic gates.

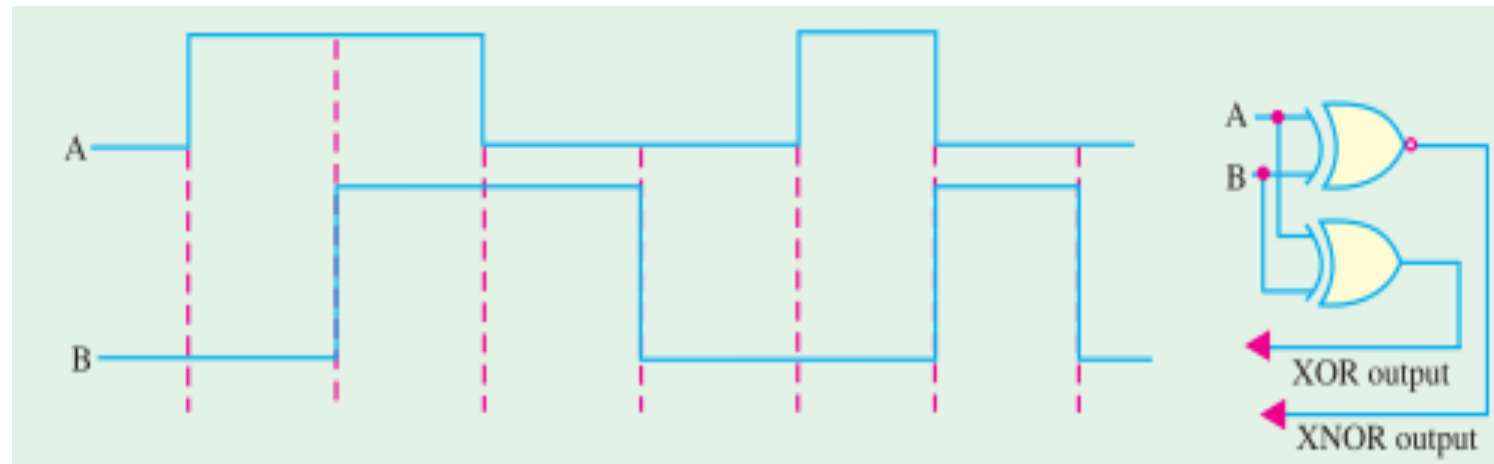

**Fig. 70.71**